

The same equations used in PA9 were the same equations used and can be seen below

$$\begin{aligned}
 V_1 &= V_{in} \\
 G_1(V_2 - V_1) + C \frac{d(V_2 - V_1)}{dt} + G_2 V_2 - I_L &= 0 \\
 V_2 - V_3 - L \frac{dI_L}{dt} &= 0 \\
 -I_L + G_3 V_3 &= 0 \\
 V_4 - \alpha I_3 &= 0 \\
 G_3 V_3 - I_3 &= 0 \\
 G_4(V_O - V_4) + G_O V_O &= 0
 \end{aligned}$$

Matrices:

$$\mathbf{C} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -C & C & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -L & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \mathbf{G} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ -G_1 & G_1 + G_2 & -1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & G_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -\alpha & 1 & 0 \\ 0 & 0 & 0 & G_3 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -G_4 & G_4 + G_O \end{bmatrix}$$

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ I_L \\ V_3 \\ I_3 \\ V_4 \\ V_O \end{bmatrix} \quad \mathbf{F} = \begin{bmatrix} V_{in} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Fig 1 Differential Equations

The DC Sweep V_{in} and V_{out} plots, along with the frequency spectrums can be seen in figures 1 to 3 below:

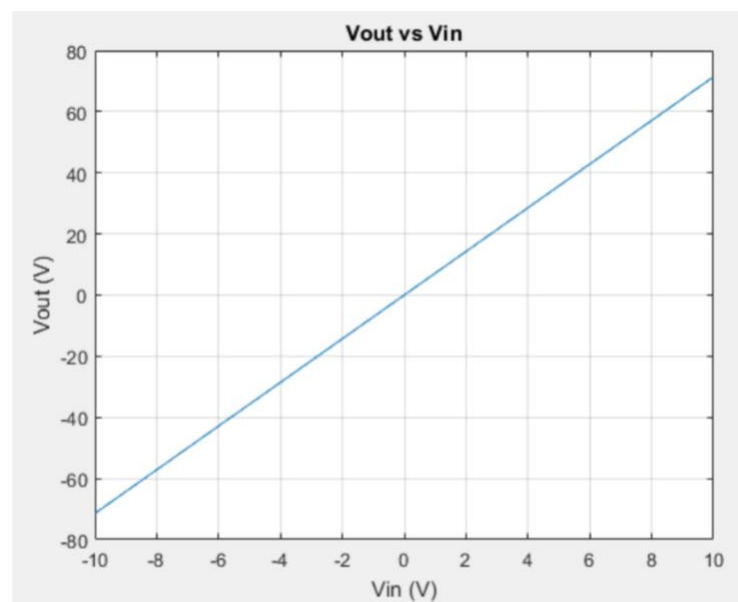


Fig 1 Vout vs Vin

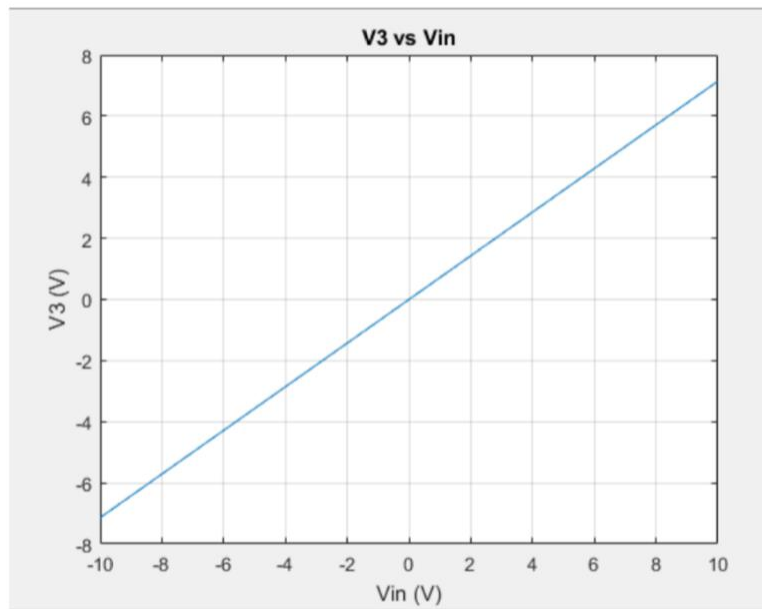


Fig 2 V3 vs Vin

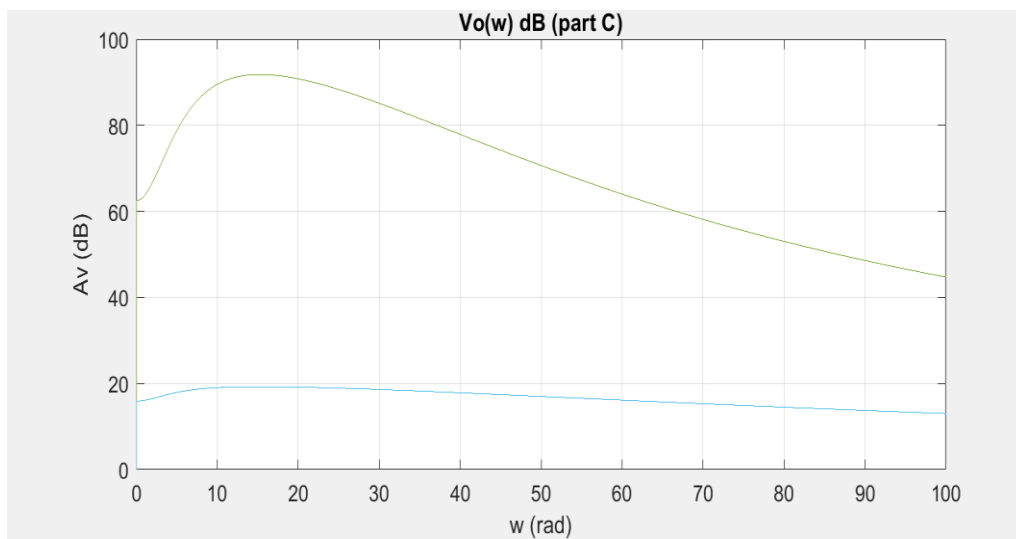


Fig 3 Ac plot of Vo as a function of w

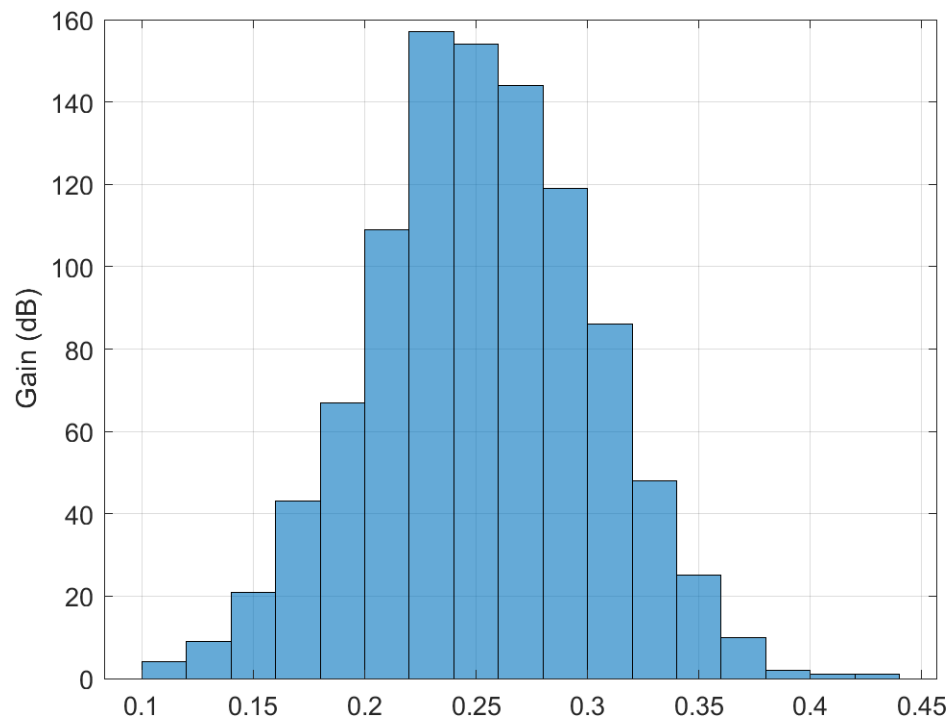


Fig 4

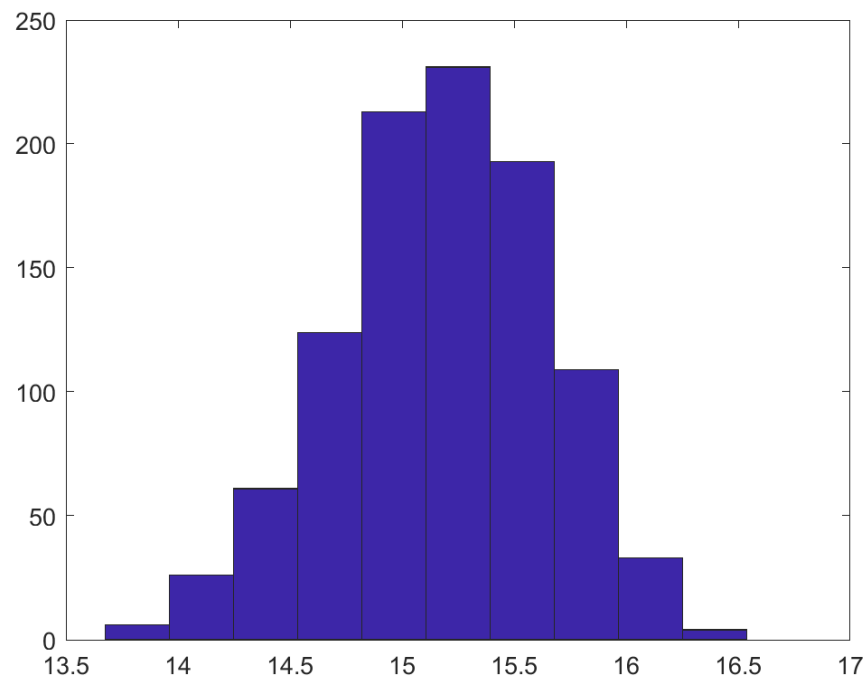


Fig 5 Histogram of Gain

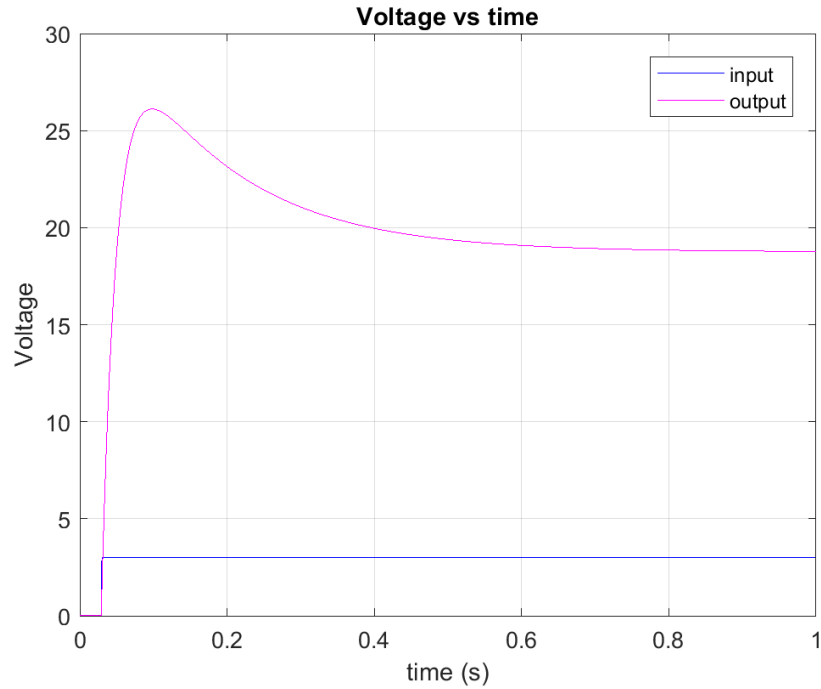


Fig 6 Plot of the Voltage vs Time

- a.) By inspection the circuit is a low pass filter
- b.) We should expect the frequency response to cut off high frequencies and allow only the low frequencies to go through.
- d.) Part v: As the time step is increased the accuracy of the simulation is decreased.

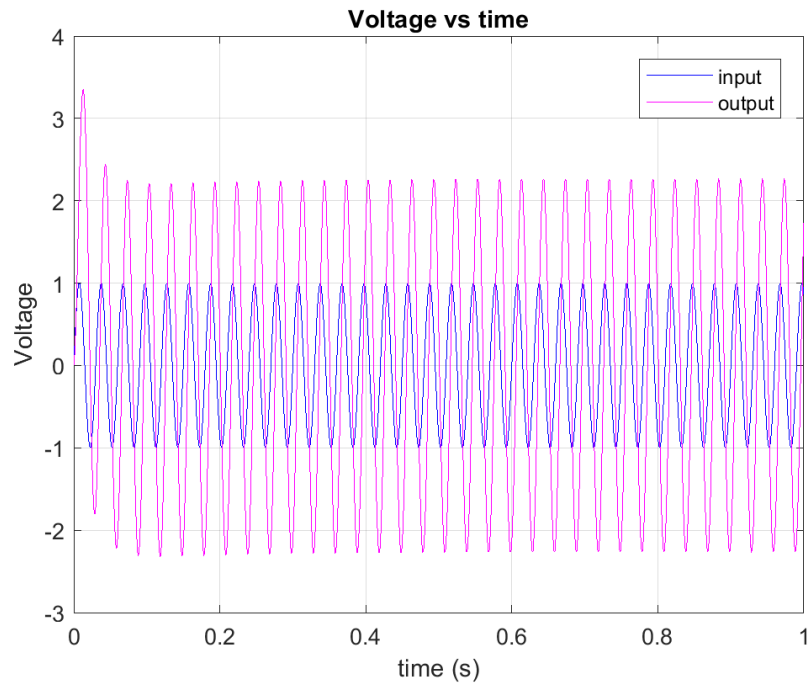


Fig 7 Voltage vs Time Input and Output siSnusoid

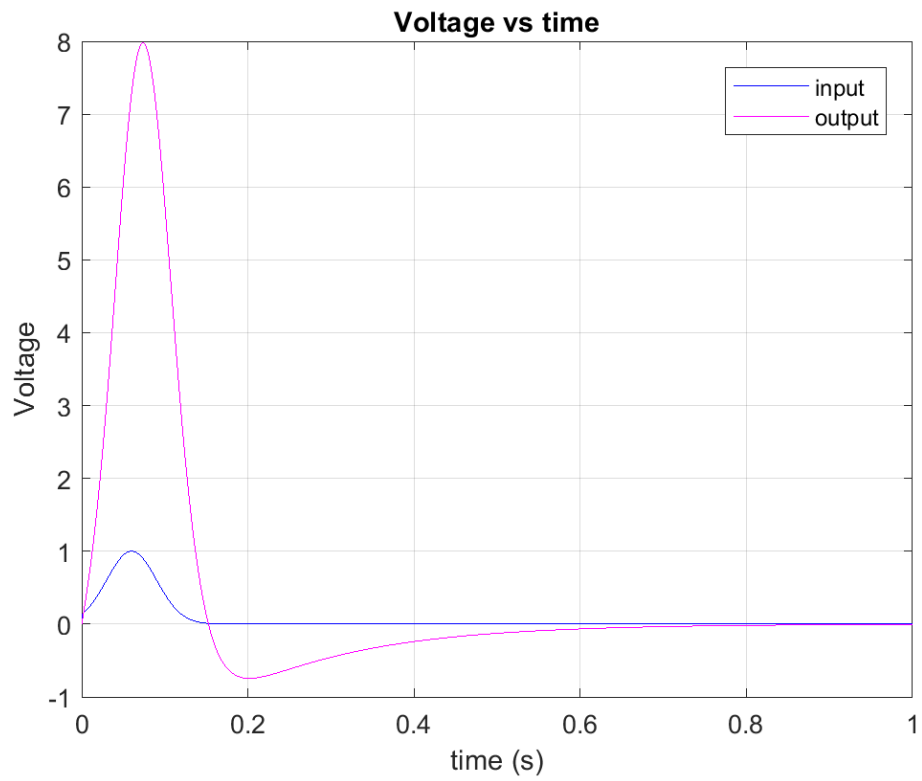


Fig 8 Voltage vs Time with Input and Output

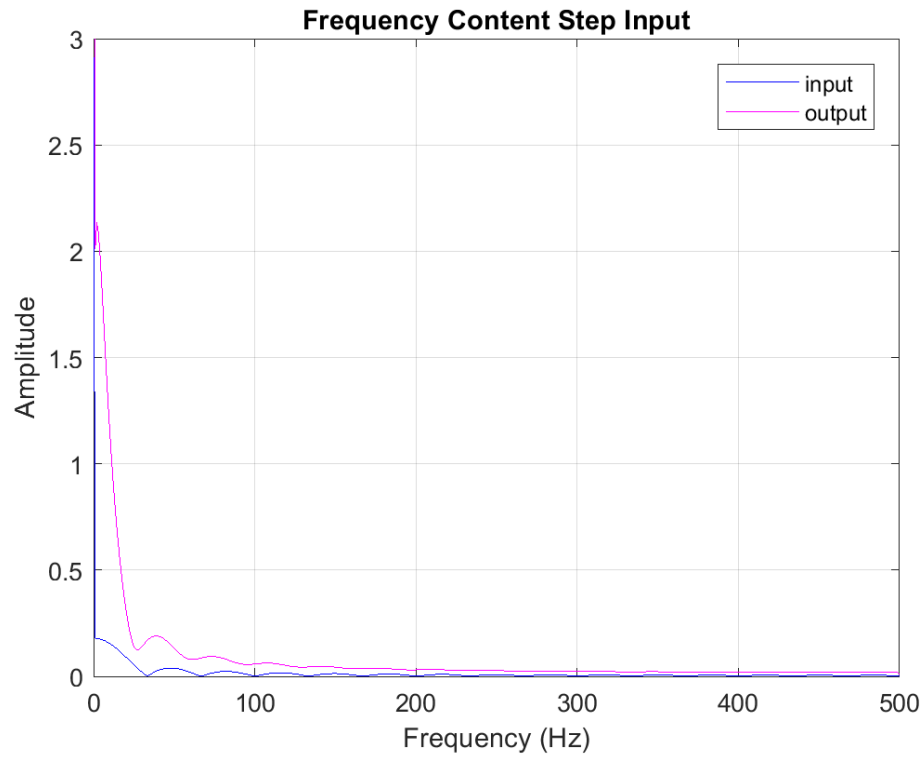


Fig 9 Frequency Content Step Input

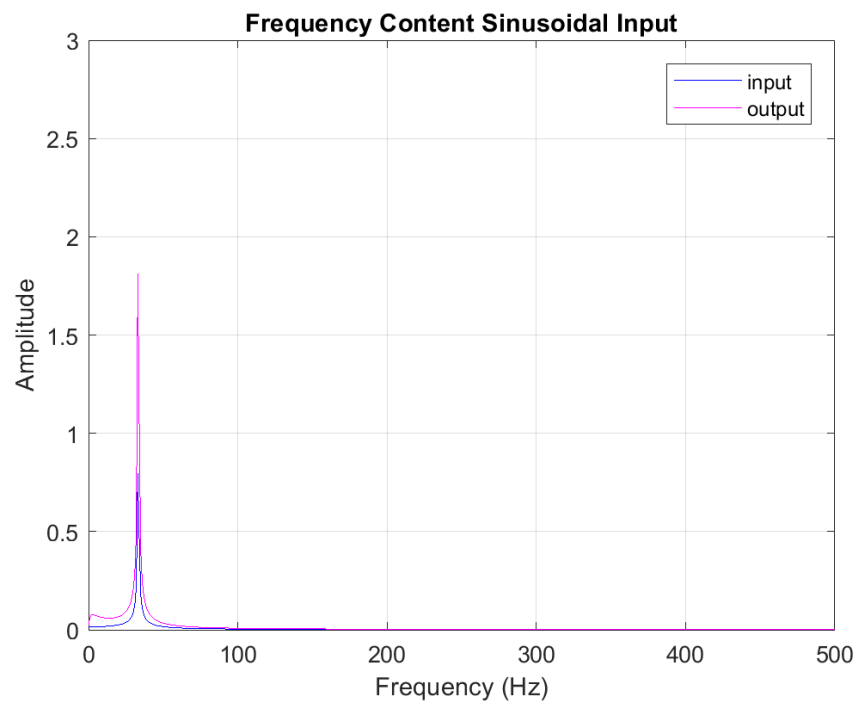


Fig 10 Frequency Content Sinusoidal Input

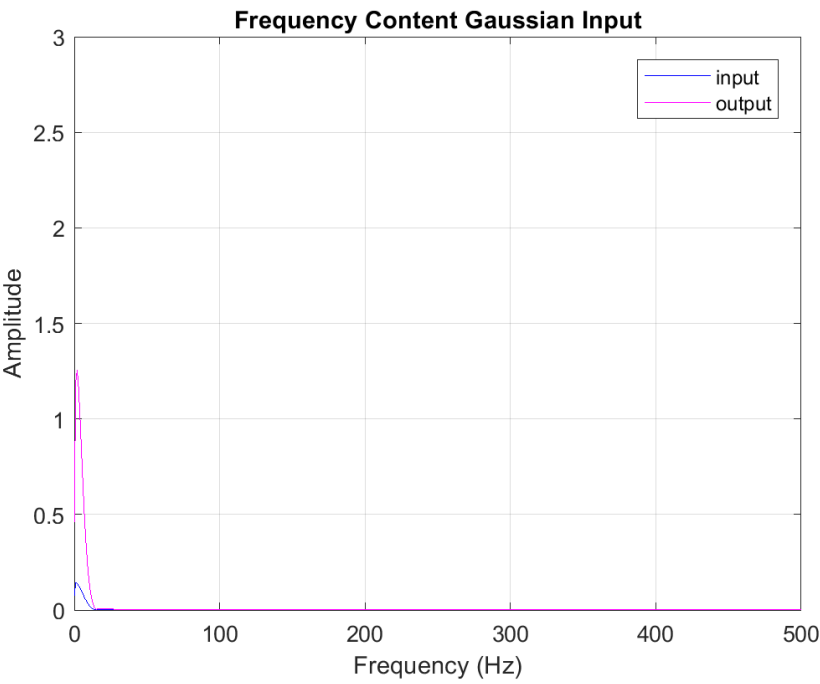


Fig 11 Frequency Content Gaussian Input

C1 =							
0.2500	-0.2500	0	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0	0
0	0	0.0000	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	-0.2000	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0

C MATRIX

Varying C_n :

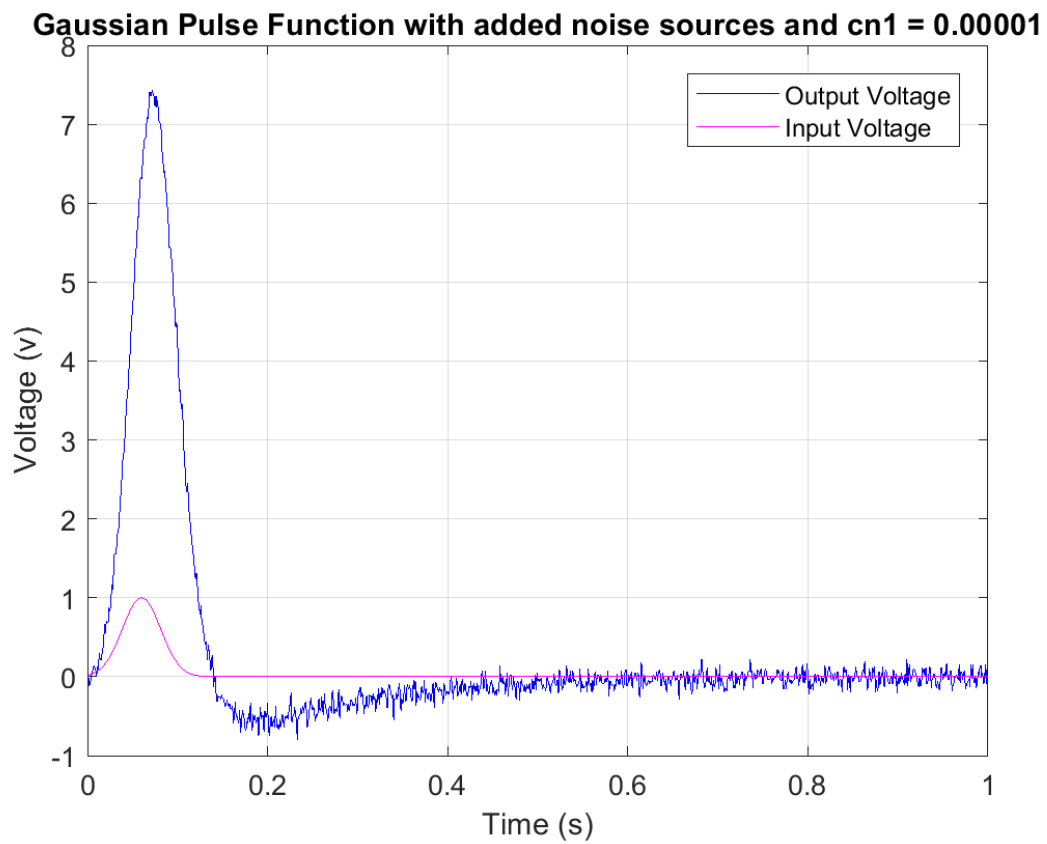


Fig 12 Gaussian Pulse Function with Added Noise $C_n = 0.00001$

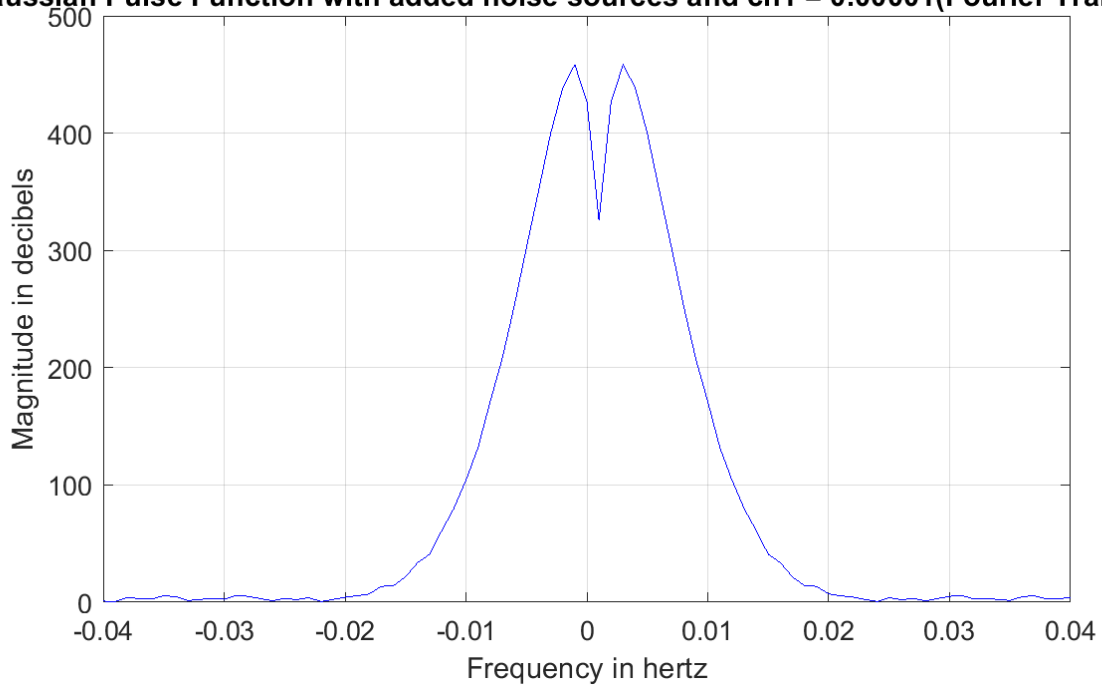
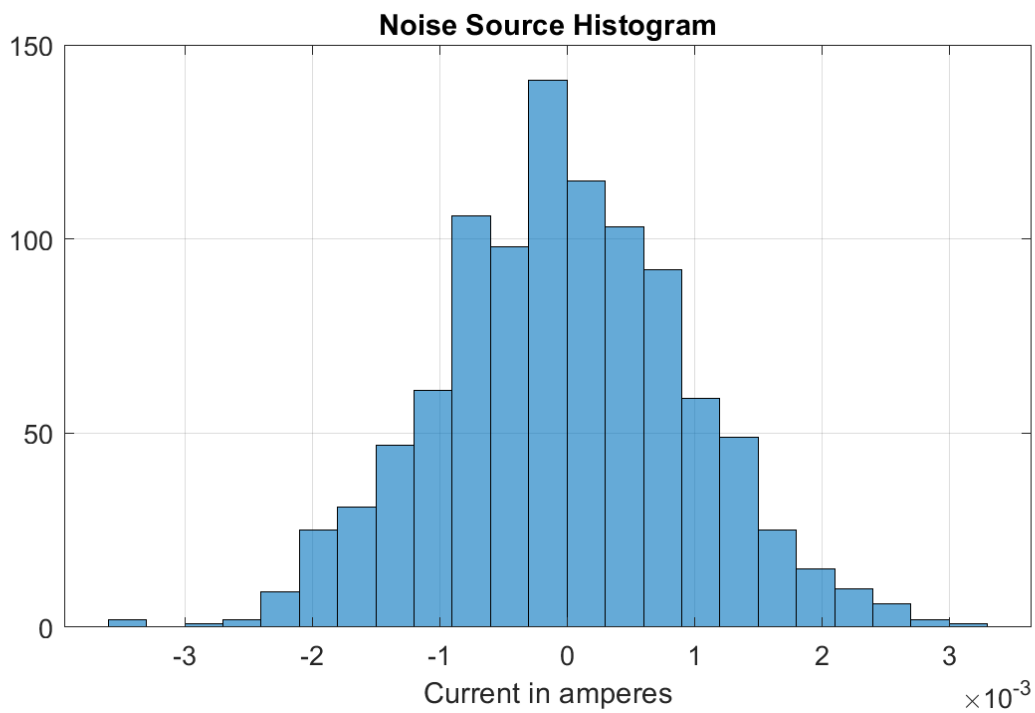
Gaussian Pulse Function with added noise sources and $cn1 = 0.00001$ (Fourier TransformFig 13 Gaussian Pulse function with added noise sources $cn1=0.00001$ 

Fig 14 Noise Source Histogram

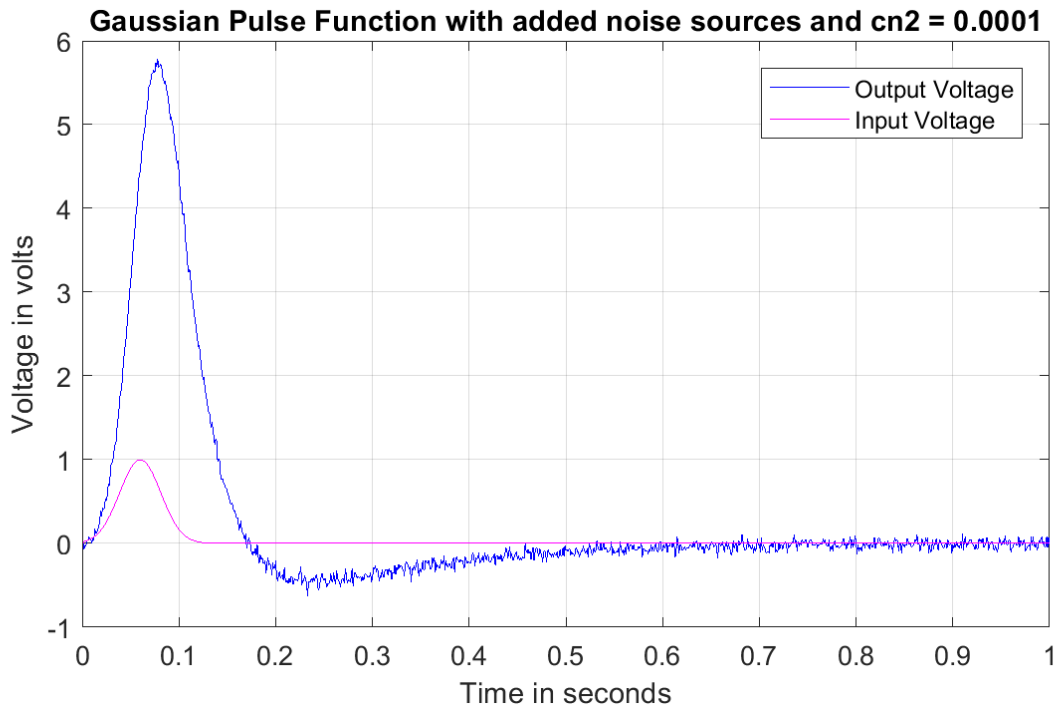
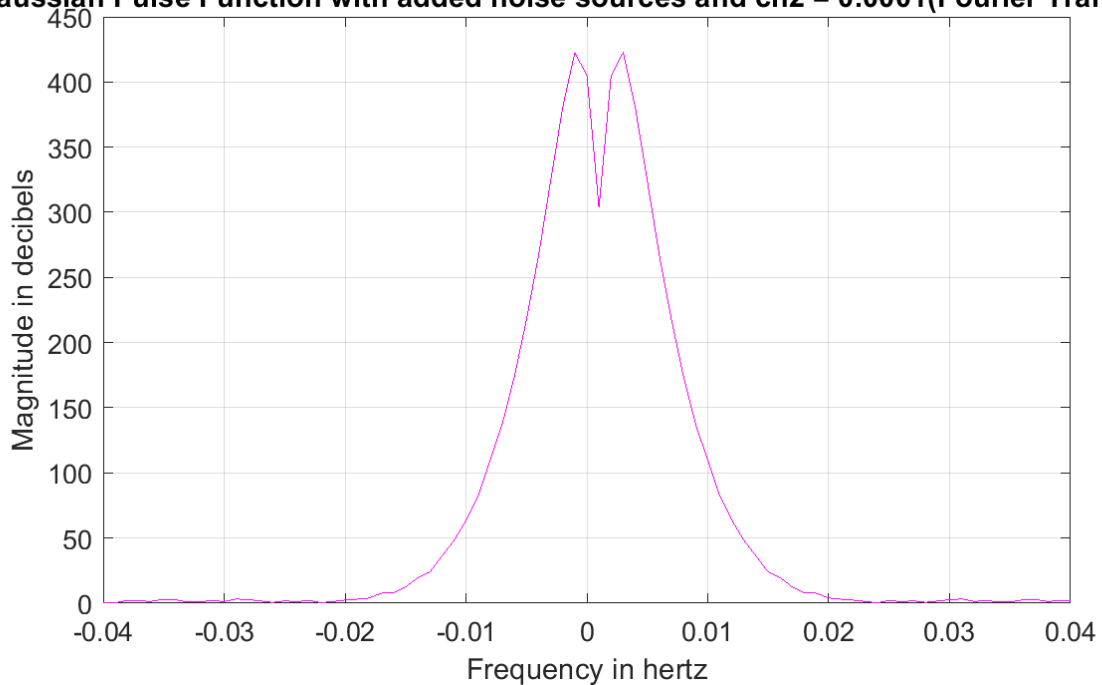
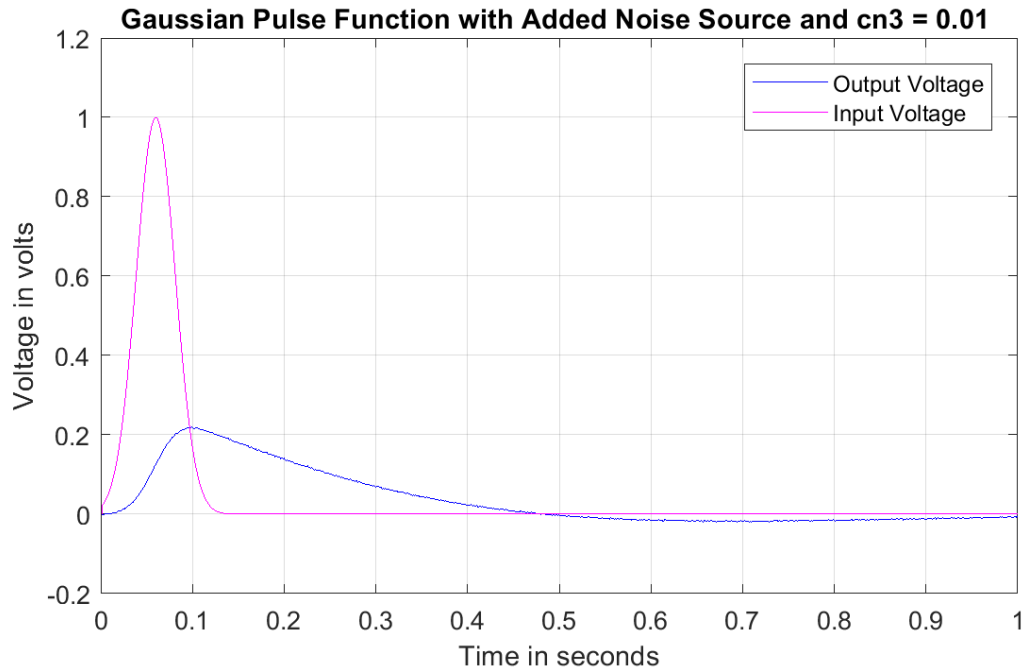
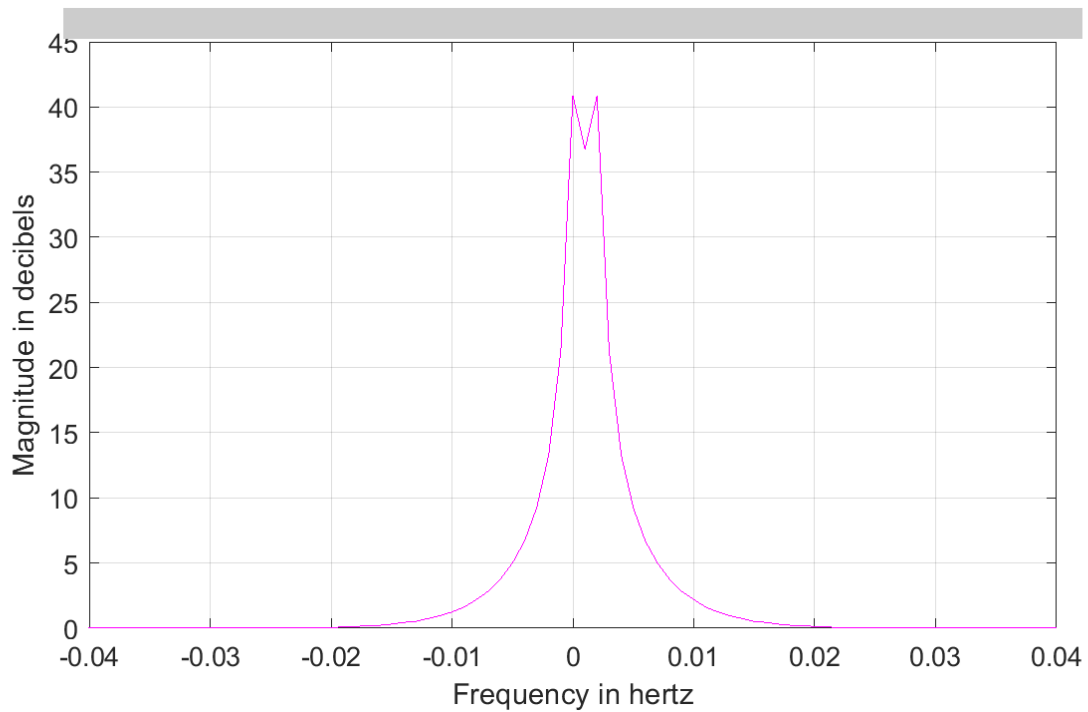


Fig 15

Gaussian Pulse Function with added noise sources and $cn2 = 0.0001$ (Fourier Transform)Fig 16 Gaussian Pulse function with added noise sources and $cn2=0.0001$

Fig 17 Gaussian Pulse function with added noise sources and $cn3=0.01$ Fig 18 Gaussian Pulse function with added noise sources and $cn3=0.01$

In the end we can see that as cn gets larger the bandwidth gets smaller.

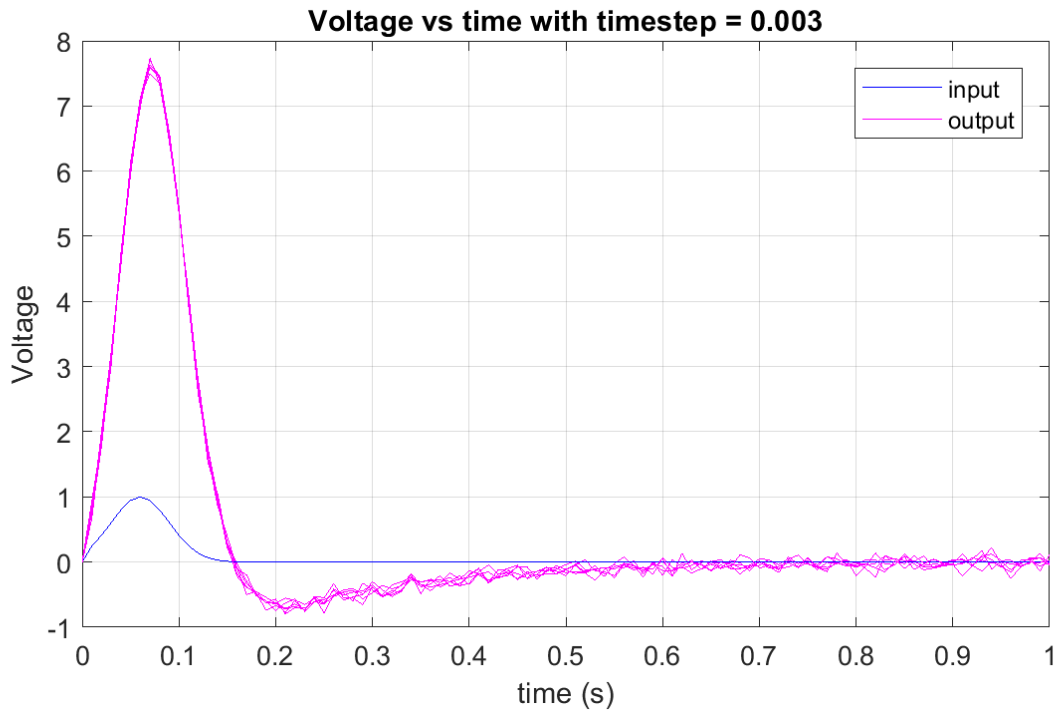


Fig 19 Plot when time step equals 0.003

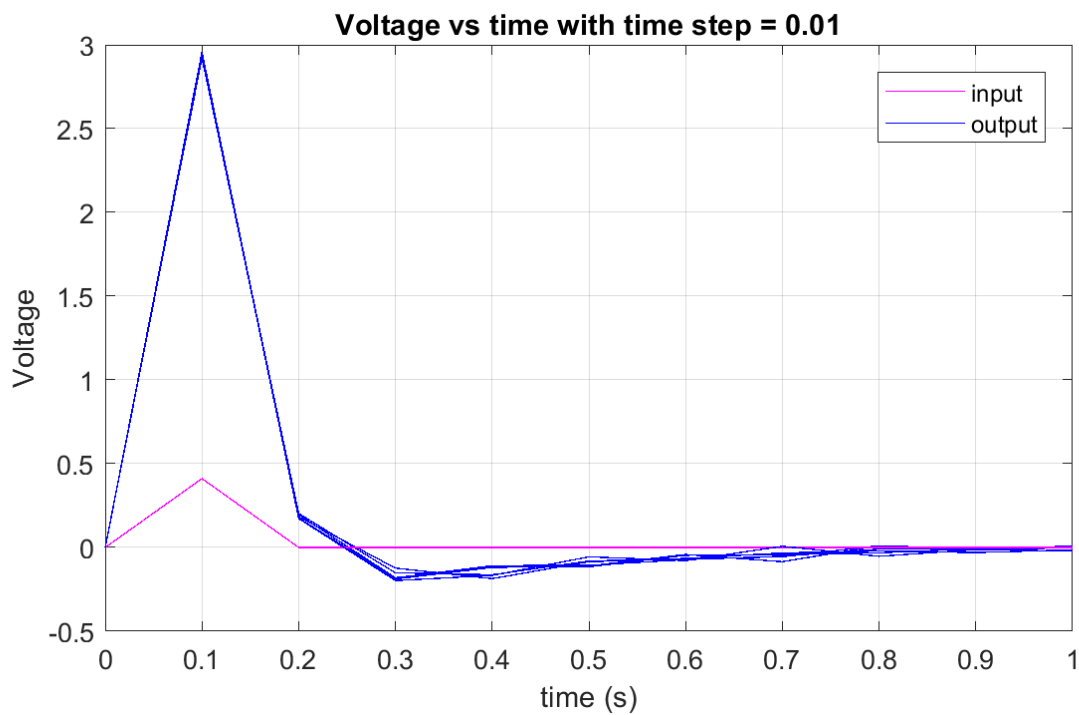


Fig 20 Plot when time step equals 0.01

What was observed was that as the time step is increased the accuracy of the simulation decreases.

Non-Linearity: In order to implement this in MATLAB another matrix is needed to represent the equations for the non-linear elements. A column vector $B(V)$ will have to be added. The current system is non-linear it can't be solved by simple Gaussian elimination and instead the newton Raphson numerical method has to be used instead